

ECE-124 Lab-4 Submission Form – Winter 2018				
GROUP NUMBER: 7		Lab4 Demo	Lab4 Report	
SESSION NUMBER: 202		Out of 10	Out of 10	
Partner A: YiFan Yu	yf3yu	<i>[Signature]</i>		
Partner B: Daguang Ruan	d2ruan	<i>Brian Ruan</i>		
<b>LAB4 DESIGN DEMO</b>		<b>Marks Allotted</b>	<b>A</b>	<b>B</b>
Target X value on Digit1 (pb3 OFF); Target Y value on Digit2 (pb2 OFF)		1	1	1
X-Motion/Y-Motion has changing values on Digit1/Digit2		1	1	1
Extender enabled only at Target co-ordinates		1	1	1
Extender Position shown on leds[7:4]		1	1	1
Grappler enabled only at Fully Extended Extender (Grappler- led[3])		1	1	1
System Error when X/Y Motion with Extender not retracted		1	1	1
System Error Cleared when Extender is retracted.		1	1	1
DISCUSSION: Comment on your VHDL Implementation?		3	3	3
<b>LAB4 DEMO MARK</b>		<b>Out of 10</b>	<b>10</b>	<b>10</b>
<b>LAB4 DESIGN REPORT (see rubric on LEARN for details)</b>		<b>Marks Allotted</b>	<b>TEAM</b>	
Structural VHDL for Top Level VHDL file (only instances and connections) – no gates except in instance input fields		2		
Simulation of 8bit Shift Register and 8 bit Binary Counter in both directions		2		
State Diagrams of Mealy SM, Moore SM1, MooreSM2 machines		2		
Mealy Form for Mealy SM; Moore form for Moore SM1, SM2		2		
Fitter Report on Resources Utilization by Entity (Logic Cells each)		2		
Delay in Report Submission (-1 per day) x number of days:				
<b>LAB4 REPORT MARK</b>		<b>Out of 10</b>		

# LAB4 GRP7 SESS202 REPORT

## VHDL SOURCE CODE 1: TOP LEVEL STRUCTURAL

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY LogicalStep_Lab4_top IS
    PORT
    (
        clk_in_50          : in    std_logic;
        rst_n              : in    std_logic;
        pb                 : in    std_logic_vector(3 downto 0);
        sw                 : in    std_logic_vector(7 downto 0); -- The switch inputs
        leds               : out std_logic_vector(7 downto 0);  -- for displaying the switch content
        seg7_data          : out std_logic_vector(6 downto 0); -- 7-bit outputs to a 7-segment
        seg7_char1         : out    std_logic;                  -- seg7
        digi_selectors     : out    std_logic;                  -- seg7
        seg7_char2         : out    std_logic;
        digi_selectors     : out    std_logic;
    );
END LogicalStep_Lab4_top;
```

ARCHITECTURE SimpleCircuit OF LogicalStep\_Lab4\_top IS

COMPONENT SevenSegment is port (

```
    hex      : in  std_logic_vector(3 downto 0);    -- The 4 bit data to be displayed
    sevenseg : out std_logic_vector(6 downto 0)      -- 7-bit outputs to a 7-segment
);
end COMPONENT;
```

COMPONENT segment7\_mux is

```
    port (
        clk      : in  std_logic := '0';
        DIN2      : in  std_logic_vector(6 downto 0);
        DIN1      : in  std_logic_vector(6 downto 0);
        DOUT      : out std_logic_vector(6 downto 0);
        DIG2      : out  std_logic;
        DIG1      : out  std_logic
    );
end COMPONENT;
```

COMPONENT MealyStatemachine IS

Port(

```
    clk_input, resetButton : IN std_logic;

    X_EQ, X_GT, X_LT : IN std_logic; --comparing DESIRED TO ACTUAL
    Y_EQ, Y_GT, Y_LT : IN std_logic; --comparing DESIRED TO ACTUAL
    extenderOut : IN std_logic;

    X_MOTION, Y_MOTION : IN std_logic;

    X_Clk_en, X_UPorDOWN: OUT std_logic;
    Y_Clk_en, Y_UPorDOWN: OUT std_logic;

    ExtenderEnable: OUT std_logic;

    isError : OUT std_logic
```

```
);
END COMPONENT;
```

COMPONENT Bin\_Counter4bit is port

```
(
    Main_clk      : in std_logic;
    rst_n         : in std_logic := '0';
    clk_en        : in std_logic := '0';
    up1_down0     : in std_logic := '0';
    counter_bits  : out std_logic_vector(3 downto 0)
);
end COMPONENT;
```

COMPONENT FourBitComparator is port (

```
    bitA0, bitA1, bitA2, bitA3, bitB0, bitB1, bitB2, bitB3 : in std_logic;

    AGTB : out std_logic;
    AEQB : out std_logic;
    ALTB : out std_logic

);
end COMPONENT;
```

COMPONENT Grappler IS Port (

```
    clk_input, rst_n, controlButton, enable : IN
std_logic;
    grappleControl : OUT std_logic
);
end COMPONENT;
```

```

COMPONENT Bidir_shift_reg is port
(
    CLK          : in std_logic := '0';
    RESET_n      : in std_logic := '0';
    CLK_EN       : in std_logic := '0';
    LEFT0_RIGHT1 : in std_logic := '0';
    REG_BITS     : OUT std_logic_vector(3 downto 0)
);
end COMPONENT;

COMPONENT Extender IS Port
(
    clk_input, rst_n, controlButton, enable           : IN
    std_logic;
    currentShiftValue
        : IN std_logic_vector(3 downto 0);
    bitShifting, extenderOut, bitShiftDirection, grapplerEnable : OUT std_logic
);
END COMPONENT;

COMPONENT mux is port (
    hex_in1, hex_in2 : in std_logic_vector(6 downto 0);
    mux_select :in std_logic;
    hex_out :      out std_logic_vector(6 downto 0)

);
end COMPONENT;

COMPONENT muxSingle is port (
    hex_in1, hex_in2 : in std_logic;
    mux_select :in std_logic;
    hex_out :      out std_logic

);
end COMPONENT;

COMPONENT FlashCounter is port
(
    Main_clk          : in std_logic;
    rst_n             : in std_logic := '0';
    clk_en            : in std_logic := '0';
    up1_down0         : in std_logic := '0';
    counter_bits      : out std_logic
);
end COMPONENT;

```

```

-----
---
    CONSTANT          SIM                                     : boolean := FALSE;
    -- set to TRUE for simulation runs otherwise keep at 0.
    CONSTANT CLK_DIV_SIZE      : INTEGER := 26;    -- size of vectors
for the counters

    SIGNAL      Main_Clk                                     : STD_LOGIC;
    -- main clock to drive sequencing of State Machine

    SIGNAL bin_counter                                     : UNSIGNED(CLK_DIV_SIZE-1 downto 0);
-- := to_unsigned(0,CLK_DIV_SIZE); -- reset binary counter to zero
-----
---

    SIGNAL XTARGET7seg, YTARGET7seg : std_logic_vector(6 downto 0);
    SIGNAL XCURRENT, YCURRENT : std_logic_vector(3 downto 0);
    SIGNAL XCURRENT7seg, YCURRENT7seg : std_logic_vector(6 downto 0);

    SIGNAL XMUX7seg, YMUX7seg: std_logic_vector(6 downto 0);

    SIGNAL XTargLTCurr, XTargEQCurr, XTargGTCurr : std_logic;
    SIGNAL YTargLTCurr, YTargEQCurr, YTargGTCurr : std_logic;

    SIGNAL bitShiftDirControl, bitShiftEnable : std_logic;
    SIGNAL currentShiftValue : std_logic_vector(3 downto 0);

    SIGNAL extenderOutSignal : std_logic;

    SIGNAL X_ClockEnable, Y_ClockEnable : std_logic;
    SIGNAL X_Direction, Y_Direction : std_logic;

    SIGNAL GrappleEnableSignal : std_logic;

    SIGNAL extenderEnableSignal : std_logic;
    SIGNAL ERROR7seg, NOTHING7seg, ERROR7segOutput : std_logic_vector(6 downto 0);
    SIGNAL X_ERROR_AND_VALUE7seg, Y_ERROR_AND_VALUE7seg:std_logic_vector(6 downto 0);

    SIGNAL ERROR : std_logic;

    SIGNAL MUX_CLOCK : std_logic;

    SIGNAL FLASH: std_logic;
-----
---
```

```

BEGIN

-- CLOCKING GENERATOR WHICH DIVIDES THE INPUT CLOCK DOWN TO A LOWER FREQUENCY

BinCLK: PROCESS(clkin_50, rst_n) is
    BEGIN
        IF (rising_edge(clkin_50)) THEN -- binary counter increments on rising clock edge
            bin_counter <= bin_counter + 1;
        END IF;
    END PROCESS;

Clock_Source:
    Main_Clk <=
    clkin_50 when sim = TRUE else
simulations only
    std_logic(bin_counter(23));
    -- for real FPGA operation

-----
--

leds (7 downto 4) <= currentShiftValue (3 downto 0);
leds (0) <= ERROR;
ERROR7seg <= "1111001";
NOTHING7seg <= "0000000";

-----
--

INST1XTARGET: SevenSegment PORT MAP (sw(7 downto 4),XTARGET7Seg);
INST2YTARGET: SevenSegment PORT MAP (sw(3 downto 0),YTARGET7Seg);
INST11XCURRENT: SevenSegment PORT MAP (XCURRENT,XCURRENT7seg);
INST12YCURRENT: SevenSegment PORT MAP (YCURRENT,YCURRENT7seg);

INST13MUX_X:mux PORT MAP (
    XCURRENT7seg, XTARGET7Seg,
    pb(3),
    XMUX7seg);

INST14MUX_Y:mux PORT MAP (
    YCURRENT7seg, YTARGET7Seg,
    pb(2),
    YMUX7seg);

INST15X_MUX_ERROR :mux PORT MAP (
    XMUX7seg, ERROR7segOutput,
    ERROR,
    X_ERROR_AND_VALUE7seg);

INST16Y_MUX_ERROR :mux PORT MAP (
    YMUX7seg,ERROR7segOutput,
    ERROR,
    Y_ERROR_AND_VALUE7seg);

INST18ERROR_AND_NOTHING: mux PORT MAP(
    ERROR7seg, NOTHING7seg,
    FLASH,
    ERROR7segOutput);

```

```

INST19FLASH: FlashCounter PORT MAP
(
    std_logic(bin_counter(23)),
    rst_n,
    '1',
    '1',
    FLASH
);

INST3: segment7_mux PORT MAP (clk_in_50, X_ERROR_AND_VALUE7seg(6 downto 0),
Y_ERROR_AND_VALUE7seg(6 downto 0), seg7_data(6 downto 0), seg7_char1, seg7_char2);

INST4X: Bin_Counter4bit PORT MAP (Main_Clk,rst_n,X_ClockEnable,X_Direction,XCURRENT(3 downto 0)
);

INST5Y: Bin_Counter4bit PORT MAP (Main_Clk,rst_n, Y_ClockEnable,Y_Direction,YCURRENT(3 downto 0)
);

INST6X: FourBitComparator PORT MAP (

    sw(4),sw(5), sw(6), sw(7),
    XCURRENT(0), XCURRENT(1), XCURRENT(2), XCURRENT(3),
    XTargGTCurr, XTargEQCurr, XTargLTCurr);

INST7Y: FourBitComparator PORT MAP (

    sw(0),sw(1), sw(2), sw(3),
    YCURRENT(0), YCURRENT(1), YCURRENT(2), YCURRENT(3),
    YTargGTCurr, YTargEQCurr, YTargLTCurr);

INST8GrapplerSM: Grappler PORT MAP (Main_Clk, rst_n, pb(0) , GrappleEnableSignal, leds(3));

INST9: Bidir_shift_reg PORT MAP(
    Main_Clk, rst_n,
    bitShiftEnable, bitShiftDirControl,
    currentShiftValue (3 downto 0) );
--
INST10: Extender PORT MAP (

    Main_Clk, rst_n, pb(1), extenderEnableSignal,
    currentShiftValue(3 downto 0),

    bitShiftEnable, extenderOutSignal, bitShiftDirControl,GrappleEnableSignal
);

INSTMEALY: MealyStatemachine PORT MAP (

    Main_Clk, rst_n,

    XTargEQCurr, XTargGTCurr, XTargLTCurr,
    YTargEQCurr, YTargGTCurr, YTargLTCurr,
    extenderOutSignal,
    pb(3), pb(2),

    X_ClockEnable, X_Direction,
    Y_ClockEnable, Y_Direction,

    extenderEnableSignal,
    ERROR

);


--INST13ERROR_MUX: mux PORT MAP (ERROR7seg,

```


```
END SimpleCircuit;
```




## Simulation 1: 8-Bits Shift Register

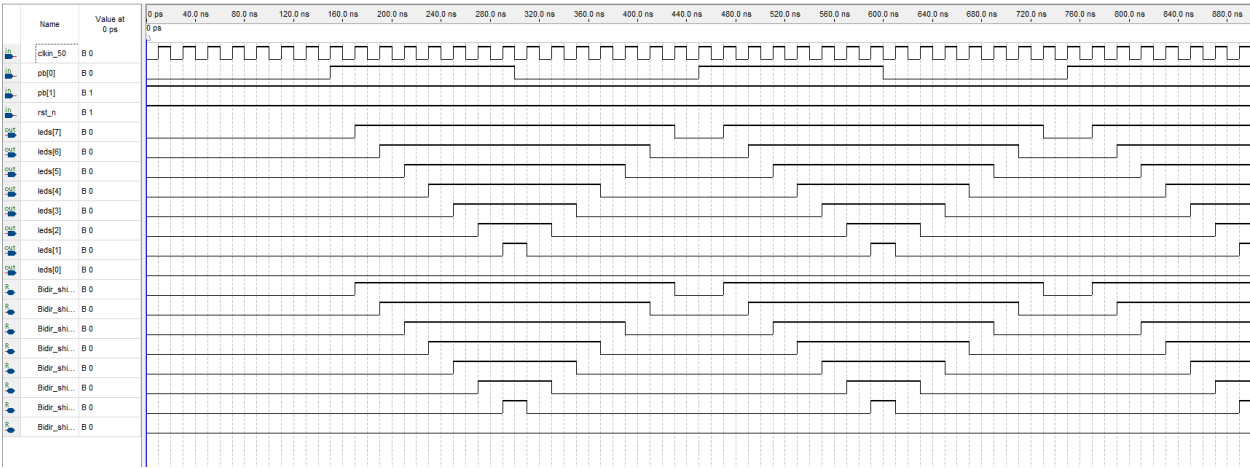


## Simulation 2: 8-Bits Counter

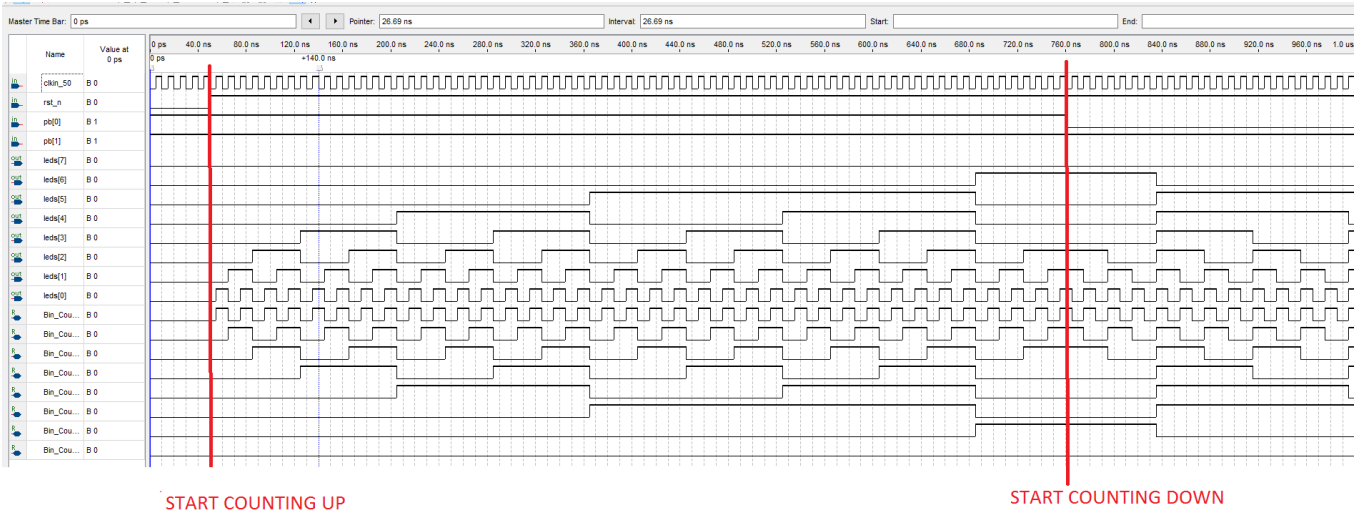


State Diagram 1 Mealy State Machine

 

 State Diagram 2: Extender Moore State Machine



 State Diagram 3: Grappler Moore State Machine



## Form of the SM

### STATE MACHINE 1: MEALY

```
] library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

Entity MealyStatemachine IS Port
(
  clk_input, resetButton : IN std_logic;

  X_EQ, X_GT, X_LT : IN std_logic; --comparing DESIRED TO ACTUAL
  Y_EQ, Y_GT, Y_LT : IN std_logic; --comparing DESIRED TO ACTUAL
  extenderOut : IN std_logic;

  X_MOTION, Y_MOTION : IN std_logic;

  X_Clk_en, X_UPorDOWN: OUT std_logic;
  Y_Clk_en, Y_UPorDOWN: OUT std_logic;

  ExtenderEnable: OUT std_logic;

  isError : OUT std_logic := '0'-- need to put that somewhere

);
END ENTITY;

Architecture behaviour of MealyStatemachine is

-- state for the X control and Y control
TYPE STATE IS (XMOVE, STOP, YMOVE, BOTHMOVE, ERROR);

SIGNAL current_state, next_state      : STATE; -- our signal for currentState and nextSate

BEGIN

-----
--State Machine:
-----

-----CONTROL FOR X-----
-- REGISTER_LOGIC PROCESS:

Register_Section: PROCESS (clk_input, resetButton, next_state)  -- this process synchronizes the
activity to a clock
BEGIN
  IF (resetButton = '0') THEN
    current_state <= STOP;

    ELSIF(rising_edge(clk_input)) THEN
      current_state <= next_State;
    END IF;
END PROCESS;
```

-- TRANSITION LOGIC PROCESS

Transition\_Section: PROCESS (current\_state, X\_EQ, X\_GT, X\_LT, Y\_EQ, Y\_GT,  
Y\_LT, extenderOut, X\_MOTION, Y\_MOTION)

BEGIN

CASE current\_state IS

--switching states depending on the value of the comparaisn  
WHEN STOP =>

IF( X\_EQ = '0' AND Y\_EQ = '0' AND (X\_MOTION='0') AND (Y\_MOTION='0')  
and extenderout = '0') THEN  
-- both are bigger or smaller AND we ve got both buttons at  
active low  
next\_state <= BOTHMOVE;  
ELSIF((X\_GT='1' or X\_LT='1') AND (X\_MOTION='0') and extenderout =  
'0' ) THEN  
next\_state <= XMOVE;  
ELSIF((Y\_GT='1' or Y\_LT='1') AND (Y\_MOTION='0') and extenderout =  
'0' ) THEN  
next\_state <= YMOVE;  
ELSIF( (X\_EQ = '0' or Y\_EQ = '0') and ((X\_MOTION='0') or  
(Y\_MOTION='0')) and extenderOut = '1') THEN  
next\_state <= ERROR;  
ELSE  
next\_state <= STOP;  
END IF;

WHEN XMOVE =>

IF( X\_EQ = '1') THEN  
next\_state <= STOP;  
ELSE  
next\_state <= XMOVE;  
END IF;

WHEN YMOVE =>

IF( Y\_EQ = '1') THEN  
next\_state <= STOP;  
ELSE  
next\_state <= YMOVE;  
END IF;

```

    WHEN BOTHMOVE =>

        IF(Y_EQ = '1' and X_EQ = '1') THEN

            next_state <= STOP;

        ELSIF( Y_EQ = '1' and X_EQ = '0') THEN

            next_state <= XMOVE;

        ELSIF( Y_EQ = '0' and X_EQ = '1') THEN

            next_state <= YMOVE;

        ELSE

            next_state <= BOTHMOVE;

        END IF;

    WHEN ERROR =>

        IF( extenderOut = '0') THEN

            next_state <= STOP;

        ELSE

            next_state <= ERROR;

        END IF;

    WHEN OTHERS =>

        next_state <= STOP;

    END CASE;

END PROCESS;

-- DECODER SECTION PROCESS

Decoder_Section: PROCESS (current_state, X_EQ, X_GT, X_LT, Y_EQ, Y_GT, Y_LT, extenderOut, X_MOTION,
Y_MOTION)

BEGIN

    CASE current_state IS

        WHEN STOP =>

            X_CLK_en <= '0';
            Y_CLK_en <= '0';
            isError <= '0';

            IF (X_EQ='1'AND Y_EQ='1') THEN

                ExtenderEnable <= '1';

            ELSE

                ExtenderEnable <= '0';

            END IF;

        WHEN XMOVE =>

            IF (X_GT='1') THEN

```

```

        X_CLK_en <= '1';
        X_UPorDOWN <= '1';

ELSIF (X_LT = '1') THEN
    -- count forward

        X_CLK_en <= '1';
        X_UPorDOWN <= '0';

ELSE
    X_CLK_en <= '0';

END IF;

WHEN YMOVE =>
    Y_CLK_en <= '0';

    IF (Y_GT='1') THEN
        -- count backward
        Y_CLK_en <= '1';
        Y_UPorDOWN <= '1';

    ELSIF (Y_LT = '1') THEN
        -- count forward
        Y_CLK_en <= '1';
        Y_UPorDOWN <= '0';

    ELSE
        Y_CLK_en <= '0';

    END IF;

WHEN BOTHMOVE =>
    IF (X_GT='1') THEN

        X_CLK_en <= '1';
        X_UPorDOWN <= '1';

    ELSIF (X_LT = '1') THEN
        -- count forward

        X_CLK_en <= '1';
        X_UPorDOWN <= '0';

    ELSE
        X_CLK_en <= '0';

    END IF;

    IF (Y_GT='1') THEN
        -- count backward
        Y_CLK_en <= '1';
        Y_UPorDOWN <= '1';

    ELSIF (Y_LT = '1') THEN
        -- count forward
        Y_CLK_en <= '1';
        Y_UPorDOWN <= '0';

```

```

ELSE
    Y_CLK_en <= '0';

END IF;

WHEN ERROR =>

    --IF ( (Y_EQ = '0' OR X_EQ = '0') AND (X_MOTION = '0' OR Y_MOTION = '0')
)THEN

    isError <= '1';
    X_CLK_en <= '0';
    Y_CLK_en <= '0';
    ExtenderEnable <= '1';
--ELSE
    --isError <= '0';

--END IF;

END CASE;

END PROCESS;

END ARCHITECTURE behaviour;

```



## STATE MACHINE 2: EXTENDER MOORE

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

Entity Extender IS Port
(
    clk_input, rst_n, controlButton, enable                                     : IN
    std_logic;
    currentShiftValue
        : IN std_logic_vector(3 downto 0);
    bitShifting, extenderOut, bitShiftDirection, grapplerEnable               : OUT std_logic
);
END ENTITY;

Architecture SM of Extender is

    TYPE STATE_NAMES IS (RETRACTED,EXTENDING1, EXTENDING2, EXTENDING3, FULLYEXTENDED); -- list all
    the STATE_NAMES values

    SIGNAL current_state, next_state      : STATE_NAMES;          -- signals of type STATE_NAMES

    BEGIN

    -----
    --State Machine:
    -----

    -- REGISTER_LOGIC PROCESS:

    Register_Section: PROCESS (clk_input, rst_n, next_state) -- this process synchronizes the
    activity to a clock
    BEGIN
        IF (rst_n = '0') THEN
            current_state <= RETRACTED;
        ELSIF(rising_edge(clk_input)) THEN
            current_state <= next_State;
        END IF;
    END PROCESS;

    -- TRANSITION LOGIC PROCESS

    Transition_Section: PROCESS ( current_state,controlButton, enable, currentShiftValue)

    BEGIN

        CASE current_state IS
            WHEN RETRACTED =>
                IF(controlButton = '0' AND enable = '1') THEN
                    next_state <= EXTENDING1;
                ELSE
                    next_state <= RETRACTED;
                END IF;

            WHEN EXTENDING1 =>
                IF(currentShiftValue = "0000") THEN
                    next_state <= EXTENDING2;
                ELSIF(currentShiftValue = "1000") THEN
```

```

        next_state <= RETRACTED;
    ELSE
        next_state <= EXTENDING1;
    END IF;

    WHEN EXTENDING2 => --forward stays here twice
        IF(currentShiftValue = "1000") THEN
            next_state <= EXTENDING3;
        ELSIF(currentShiftValue = "1110") THEN
            next_state <= EXTENDING1;
        ELSE
            next_state <= EXTENDING2;
        END IF;

    WHEN EXTENDING3 =>
        IF(currentShiftValue = "1110") THEN
            next_state <= FULLYEXTENDED;
        ELSIF(currentShiftValue = "1111") THEN
            next_state <= EXTENDING2;
        ELSE
            next_state <= EXTENDING3;
        END IF;

    WHEN FULLYEXTENDED =>
        IF(controlButton = '0' AND enable = '1' ) THEN
            next_state <= EXTENDING3;
        ELSE
            next_state <= FULLYEXTENDED;
        END IF;

        WHEN OTHERS =>
            next_state <= RETRACTED;
        END CASE;
    END PROCESS;

-- DECODER SECTION PROCESS

Decoder_Section: PROCESS ( current_state,controlButton, enable, currentShiftValue)
BEGIN
    CASE current_state IS
        WHEN RETRACTED =>
            bitShifting <= '0';
            extenderOut<= '0';
            grapplerEnable <= '0';
            bitShiftDirection <= '1';

        WHEN EXTENDING1 =>
            bitShifting <= '1';
            extenderOut<= '1';
            grapplerEnable <= '0';

        WHEN EXTENDING2 =>
            bitShifting <='1';
            extenderOut<= '1';
            grapplerEnable <= '0';

        WHEN EXTENDING3 =>
            bitShifting <= '1';
            extenderOut<= '1';
            grapplerEnable <= '0';

        WHEN FULLYEXTENDED =>
            bitShifting <= '0';
            extenderOut<= '1';
            grapplerEnable <= '1';
            bitShiftDirection <= '0';
    
```

```
        WHEN others =>
            bitShifting <= '0';
            extenderOut<= '0';
            grapplerEnable <= '0';
            bitShiftDirection <= '1';

        END CASE;
    END PROCESS;

END ARCHITECTURE SM;
```

## STATE MACHINE 3: GRAPPLER MOORE

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

Entity Grappler IS Port
(
    clk_input, rst_n, controlButton, enable                : IN std_logic;
    grappleControl                                          : OUT std_logic
);
END ENTITY;

Architecture STATEMACHINE of Grappler is

    TYPE STATE_NAMES IS (STOP, GRAPPLE);  -- list all the STATE_NAMES values

    SIGNAL current_state, next_state      : STATE_NAMES;      -- signals of type STATE_NAMES

    BEGIN

        -----
        --State Machine:
        -----

        -- REGISTER_LOGIC PROCESS:

        Register_Section: PROCESS (clk_input, rst_n, next_state)  -- this process synchronizes the
        activity to a clock
        BEGIN
            IF (rst_n = '0') THEN
                current_state <= STOP;
            ELSIF(rising_edge(clk_input)) THEN
                current_state <= next_State;
            END IF;
        END PROCESS;

        -- TRANSITION LOGIC PROCESS

        Transition_Section: PROCESS (current_state,controlButton, enable)

        BEGIN
            CASE current_state IS
                WHEN STOP =>
                    IF( controlButton = '0' AND enable= '1' ) THEN --pressed
                        next_state <= GRAPPLE;

                    ELSE
                        next_state <= STOP;
                    END IF;

                WHEN GRAPPLE =>
                    IF( controlButton = '0' OR enable= '0') THEN --pressed
                        next_state <= STOP;
                    ELSE
                        next_state <= GRAPPLE;
                    END IF;

            WHEN OTHERS =>
                next_state <= STOP;
            END CASE;
        END PROCESS;
    END ARCHITECTURE;
```

```

END PROCESS;

-- DECODER SECTION PROCESS

Decoder_Section: PROCESS (current_state, controlButton, enable)
BEGIN
    CASE current_state IS
        WHEN STOP =>

            grappleControl <= '0';

        WHEN GRAPPLE =>

            grappleControl <= '1';

        WHEN others =>

            grappleControl <= '0';

    END CASE;
END PROCESS;

END ARCHITECTURE STATEMACHINE;

```

Difference between a Mealy and a Moore

The output of a Mealy machine is dependent on both the input and the current state while the output of a Moore machine is only dependent on the current state.

## Fitter Report on Resources Utilization by Entity

Fitter Resource Utilization by Entity					
	Compilation Hierarchy Node	Logic Cells	Dedicated Logic Registers	I/O Registers	Memory Bits
1	▼  LogicalStep_Lab4_top	153 (25)	48 (24)	0 (0)	0
1	Bidir_shift_reg:INST9	4 (4)	4 (4)	0 (0)	0
2	Bin_Counter4bit:INST4X	7 (7)	4 (4)	0 (0)	0
3	Bin_Counter4bit:INST5Y	6 (6)	4 (4)	0 (0)	0
4	Extender:INST10	16 (16)	5 (5)	0 (0)	0
5	FlashCounter:INST19FLASH	1 (1)	1 (1)	0 (0)	0
6	FourBitComparator:INST6X	6 (6)	0 (0)	0 (0)	0
7	FourBitComparator:INST7Y	4 (4)	0 (0)	0 (0)	0
8	Grappler:INST8GrapplerSM	2 (2)	1 (1)	0 (0)	0
9	MealyStatemachine:INSTMEALY	34 (34)	5 (5)	0 (0)	0
10	SevenSegment:INST11XCURRENT	7 (7)	0 (0)	0 (0)	0
11	SevenSegment:INST12YCURRENT	7 (7)	0 (0)	0 (0)	0
12	SevenSegment:INST1XTARGET	7 (7)	0 (0)	0 (0)	0
13	SevenSegment:INST2YTARGET	7 (7)	0 (0)	0 (0)	0
14	segment7_mux:INST3	22 (22)	0 (0)	0 (0)	0